

Question				Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
4	(a)	(i)		$300 + 50 = 350 \text{ } [\Omega]$		1		1	1	1
		(ii)		7 [V]	1			1		1
		(iii)		Substitution $I = \frac{V}{R} = \frac{7 \text{ ecf}}{350 \text{ ecf}} \text{ (1)}$ $= 0.02 \text{ [A]} \text{ (1)}$	1	1		2	2	2
		(iv)		Must match previous answer expect: 0.02 [A]	1			1		1
	(b)			temperature (1) decreases (1) increases (1)	1	1 1		3		3
	(c)	(i)		Use a {light dependent resistor / LDR}			1	1		1
		(ii)		Its <u>resistance</u> changes with [different] light [levels] OR it has high <u>resistance</u> in the dark OR it has low <u>resistance</u> in the light			1	1		1
				Question 4 total	4	4	2	10	3	10