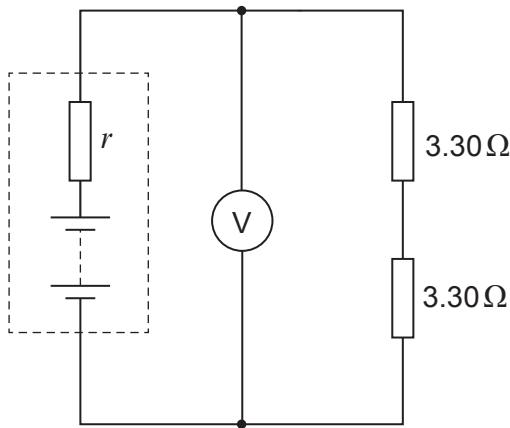


Answer all questions.

1. (a) Two $3.30\,\Omega$ resistors are connected in series across a battery of emf $4.80\,\text{V}$ as shown. The voltmeter reads $4.33\,\text{V}$.

Diagram 1



- (i) State in terms of work or energy what is meant by the emf of a battery. [2]

.....

.....

.....

- (ii) Show that the internal resistance, r , of the battery is approximately $0.7\,\Omega$. [2]

.....

.....


.....

.....

.....

- (iii) When the resistors are connected in parallel as shown below, the voltmeter reads $3.35\,\text{V}$.

Diagram 2

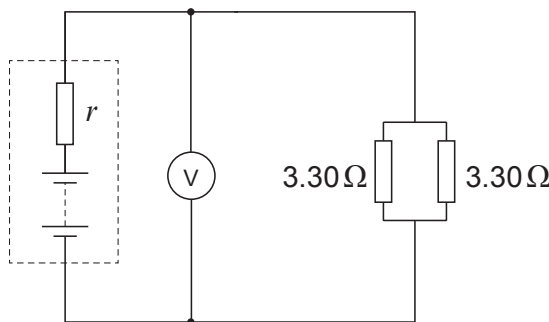

Examiner
only

(I) **Without further calculation** explain why you would expect the reading to be lower, now that there is a lower resistance across the cell terminals. [2]

.....

.....

.....

.....

.....

(II) Calculate the number of electrons entering **either** of the resistors (shown in Diagram 2) per **minute**. [3]

.....

.....

.....

.....

.....

(b) The heating element (a coil of wire) in an electric heater dissipates energy at a rate of 1.00 kW, when connected across the 230 V mains supply. Calculate:

(i) the resistance of the coil; [2]

.....

.....

.....

.....

(ii) the energy dissipated per hour, giving your answer in megajoules (MJ). [1]

.....

.....

.....

2420U201
03



Examiner
only

- (c) For each megajoule of heat from an electric heater, approximately 0.08 m^3 of gas would have to be burned in a gas-fired electricity power station. For each megajoule of heat from a domestic gas fire or boiler, approximately 0.03 m^3 of gas is burned. Discuss whether the use of electric heaters in houses should be discouraged. Calculations are not required. [3]

.....

.....

.....

.....

.....

.....

.....

.....

15

