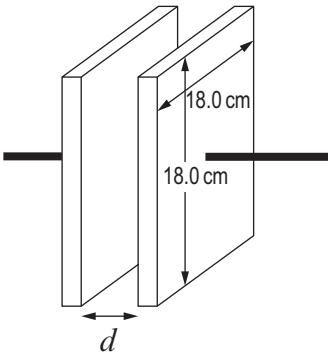


SECTION A

Answer all questions.

1. (a) (i) A laboratory technician has two square aluminium plates with sides of length 18.0 cm. Calculate the separation, d , of the plates that produces a capacitance of 2.0 nF. [3]



.....


.....

.....

.....

.....

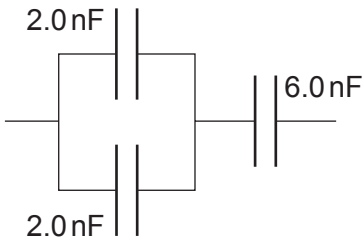- (ii) Calculate the capacitance of the capacitor combination shown. [3]



.....

.....

.....


.....

.....



Examiner
only

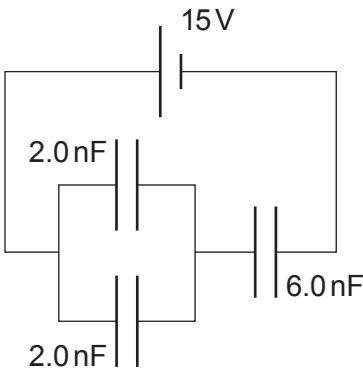(iii) Show that the charge stored on a 2.0 nF capacitor in the following circuit is 18 nC . [3]



.....

.....

.....

.....

.....

.....

(iv) Calculate the total energy stored by the capacitor combination. [2]

.....

.....

.....


.....




Examiner
only

(b) A group of students investigated the **charging** of a capacitor through a resistor and obtained the following data.

pd across capacitor / V

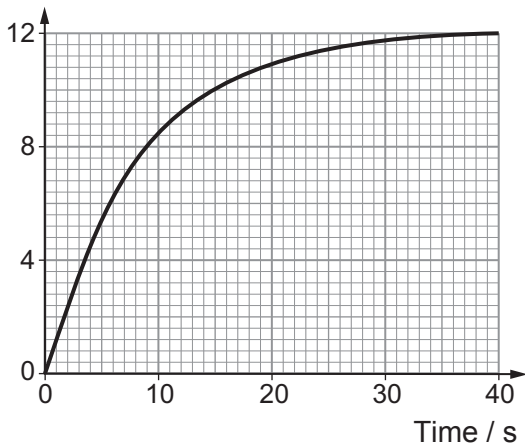

Current / mA

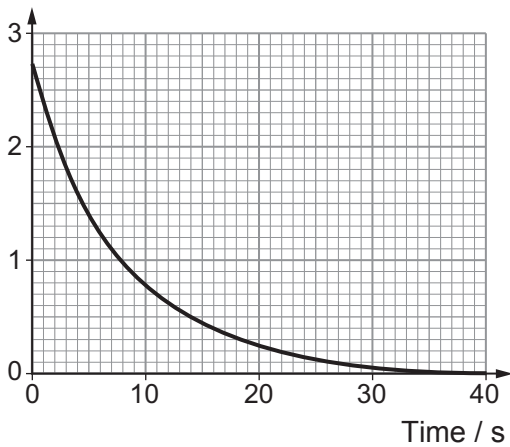

(i) Draw a circuit diagram of the apparatus that might have been used to obtain the data. [2]

(ii) Use the graphs to determine:

- the emf of the power supply;
- the resistance of the resistor;
- the capacitance of the capacitor.

[5]

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

