

2. Describe how you would carry out an experiment to investigate the discharging of a capacitor through a resistor to determine the time constant. [6 QER]

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

