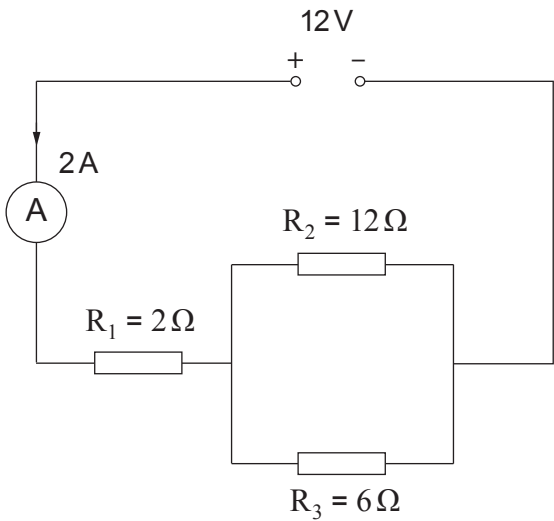


Examiner
only

3. A group of students set up the following circuit. Their aim is to measure the current through the ammeter and to use it to calculate the currents and voltages in the various parts of the circuit.



Use an equation(s) from page 2 to answer the following questions.

- (i) Calculate the voltage across R_1 . [2]

Voltage = V

- (ii) Use your answer to part (i) to calculate the current through each of the parallel resistors. [4]

Current through R_2 = A

Current through R_3 = A

6

