

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
		(iii)	For $40\ \Omega$, power $[= I^2 R = 0.3^2 \times 40] = 3.6\ \text{[W]} (1)$ Power from parallel arrangement $= [I^2 R = 0.3^2 \times 8] = 0.72\ \text{[W]} (1)$ Alternative for the first 2 marks Correct use of IV or $\frac{V^2}{R}$ Third mark: $\frac{3.6}{0.72} [= 5]$ or $\frac{0.72}{3.6} = [\frac{1}{5}] (1)$ Alternative: $\frac{2.4}{12}$ or $\frac{8}{40} (1)$ $= \frac{1}{5} (1)$ Because current is the same or equivalent (1)		3		3	3	
			Question 2 total	5	11	0	16	8	0