

Question				Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
3	(b)	(iii)		{Parallel combination / total circuit} resistance increases or main current decreases (1) So greater [proportion of 12] V across parallel combination or smaller pd across r or pd across battery terminals increases (1) So for $20\ \Omega$ resistor, pd is greater or current is greater, so Dafydd is correct (1) No argument that doesn't involve r is valid, but give 1 mark for greater [proportion than before of] current goes through the $20\ \Omega$			3	3		
				Question 3 total	5	6	3	14	4	0