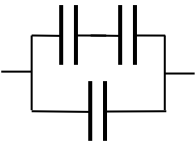
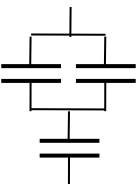


Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
4	(a)		Substitution into: $C = \frac{\epsilon_0 A}{d}$ (1) Correct answer = 1.24 n[F] (1)	1	1		2	1	
	(b)	(i)	Combining $0.5QV$ and $Q = CV$ (or using $0.5CV^2$) (1) Correct answer = 20 [V] (1)		2		2	2	
		(ii)	2 capacitors in series all in parallel with another  Allow 1 mark for  Subtract a mark if the symbol for capacitor is wrong			2	2	2	