

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
	(c)	(i)	Answer = 152 m[A]		1		1	1	
		(ii)	Correct angular frequency obtained (28 072) OR $f_0 = 4468$ [Hz] OR $2 \times f_0 = 8932$ [Hz] (1) Correct use of impedance equation i.e. 1140 [Ω] (1) Rearrangement of $I = \frac{V}{Z}$ (1) ecf on Z Correct answer = 11 m[A] (1)		4		4	4	
	(d)		Multiplying 240 [mV] by $\sqrt{2}$ [= 339 [mV]] (1) Dividing by y -sensitivity (ecf on 240) (1) Using $T = \frac{1}{f}$ ($14.8 \mu\text{s}$) (1) Dividing by time div (7.4 squares) (1) Time base good (one and $1/3$ wave ok) AND y -sensitivity gives too small a height (independent mark & may well imply the other 4 marks if seen alone) (1)			5	5	2	
			Question 7 total	6	9	5	20	10	0