

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
		(ii)		Resistance of the thermistor increases (1) So current [through the thermistor] decreases (1) But current through the resistor is unchanged (1) So she is (partially) wrong / correct for one but not the other To award full marks the conclusion must be present			3	3		3
				Question 4 total	3	8	3	14	9	14