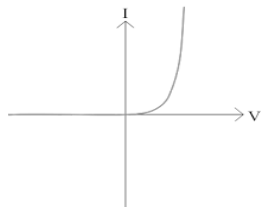


Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
	(d)	(i)		Connect in series one way and see if lamp lights or the resistance will be low or current will be high (1) Reverse the cell / battery / + and - / connection / box (1) See if the lamp still lights or the resistance will be much higher or diode only lets current flow one way or current will be zero (very small) (1) Alternative: Replace lamp with sealed box / add in series [with lamp] (1) Vary R and take series of reading of current and voltage (1) Reverse box / polarity of cell and repeat step 2 (1)			3	3		3
		(ii)		 Don't accept S shapes or curve with a decreasing gradient	1			1		1
				Question 1 total	4	5	6	15	6	15