

Question				Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
3	(a)	(i)		24 [Ω]		1		1		
		(ii)		Substitution: current = $\frac{12}{24}$ ecf (1) = 0.5 [A] (1)	1	1		2	2	
		(iii)		Substitution: power = 0.5 ecf $\times$ 12 (1) = 6 [W] (1)	1	1		2	2	
	(b)	(i)		LED selected so tick in box 2	1			1		
		(ii)	I	8 [mA]		1		1		
			II	16 [mA] ecf i.e. 8 + answer from the previous part		1		1		
		(iii)	I	L ₂ and L ₃	1			1		
			II	L ₁ and L ₂ or L ₁ and L ₃	1			1		
				Question 3 total	5	5	0	10	4	0