

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
6			Indicative content 1. Adjust the variable resistor. 2. Use the ammeter to measure the current. 3. Use the voltmeter to measure the voltage. 4. Record the readings of voltage and current. 5. Repeat steps 1 to 4 {for the full range of the variable resistor / to give several pairs of readings}. 6. Plot a graph of current (y-axis) against voltage (x-axis). 5 – 6 marks Detailed account of method. <i>There is a sustained line of reasoning which is coherent, relevant, substantiated and logically structured. The candidate uses appropriate scientific terminology and accurate spelling, punctuation and grammar.</i> 3 – 4 marks Partial account of method. <i>There is a line of reasoning which is partially coherent, largely relevant, supported by some evidence and with some structure. The candidate uses mainly appropriate scientific terminology and some accurate spelling, punctuation and grammar.</i>	6			6		6