

| Question |     |      |     | Marking details                                                                                                                                                                                                                                                                                  | Marks available |     |     |       |       |      |
|----------|-----|------|-----|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|-----|-----|-------|-------|------|
|          |     |      |     |                                                                                                                                                                                                                                                                                                  | AO1             | AO2 | AO3 | Total | Maths | Prac |
| 3        | (a) | (i)  |     | <u>12 J</u> transferred [from chemical to electrical or work done] (1)<br>per {unit charge / coulomb} [passing through cell] (1)                                                                                                                                                                 | 2               |     |     | 2     |       |      |
|          |     | (ii) |     | pd drops below emf<br><b>or</b> energy is wasted inside cell<br><b>or</b> the internal resistance limits the current [that the battery can deliver]                                                                                                                                              |                 | 1   |     | 1     |       |      |
|          | (b) | (i)  | I.  | 7.0 V across parallel combination <b>or</b> $R = 20\ \Omega \times \frac{0.35\ \text{A}}{0.25\ \text{A}}$ <b>or</b> by implication (1)<br>$R = \left[ \frac{7.0\ \text{V}}{0.25\ \text{A}} \right] = 28\ [\Omega]$ (1)                                                                           |                 | 2   |     | 2     | 1     |      |
|          |     |      | II. | 5.0 V across $r$ <b>ecf or</b> resistance of parallel combi = 11.7 $\Omega$ <b>ecf and</b> total resistance in circuit = 20.0 $\Omega$ <b>ecf or</b> by implication (1)<br>$r = \left[ \frac{5.0\ \text{V}}{0.60\ \text{A}} \right] = 8.3\ [\Omega]$ (1)                                         |                 | 2   |     | 2     | 1     |      |
|          |     | (ii) | I.  | $0.35^2 \times 20$ (1)<br>$\times 40 \times 60$ [= 5.9 kJ or 5880 J] (1)<br><b>Alternative:</b><br>$0.35 \times 7$ <b>ecf</b> (1)<br>$\times 40 \times 60$ [= 5.9 kJ or 5880 J] (1)<br><b>Alternative:</b><br>$\frac{7^2 \text{ ecf}}{20}$ (1)<br>$\times 40 \times 60$ [= 5.9 kJ or 5880 J] (1) | 1               | 1   |     | 2     | 2     |      |
|          |     |      | II. | From electrical (accept KE of electrons) into random <b>or</b> vibrational <b>or</b> thermal <b>or</b> internal (accept heat) (1)<br>[Free] electrons collide with {ions / atoms / lattice} (1)                                                                                                  | 2               |     |     | 2     |       |      |

| Question |     |       |  | Marking details                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                        | Marks available |     |     |       |       |      |
|----------|-----|-------|--|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|-----|-----|-------|-------|------|
|          |     |       |  |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                        | AO1             | AO2 | AO3 | Total | Maths | Prac |
| 3        | (b) | (iii) |  | <p>{Parallel combination / total circuit} resistance increases <b>or</b> main current decreases (1)<br/>So greater [proportion of 12] V across parallel combination <b>or</b> smaller pd across <math>r</math><br/><b>or</b> pd across battery terminals increases (1)<br/>So for <math>20\ \Omega</math> resistor, pd is greater <b>or</b> current is greater, so Dafydd is correct (1)</p> <p>No argument that doesn't involve <math>r</math> is valid, but give 1 mark for greater [proportion than before of] current goes through the <math>20\ \Omega</math></p> |                 |     | 3   | 3     |       |      |
|          |     |       |  | Question 3 total                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       | 5               | 6   | 3   | 14    | 4     | 0    |