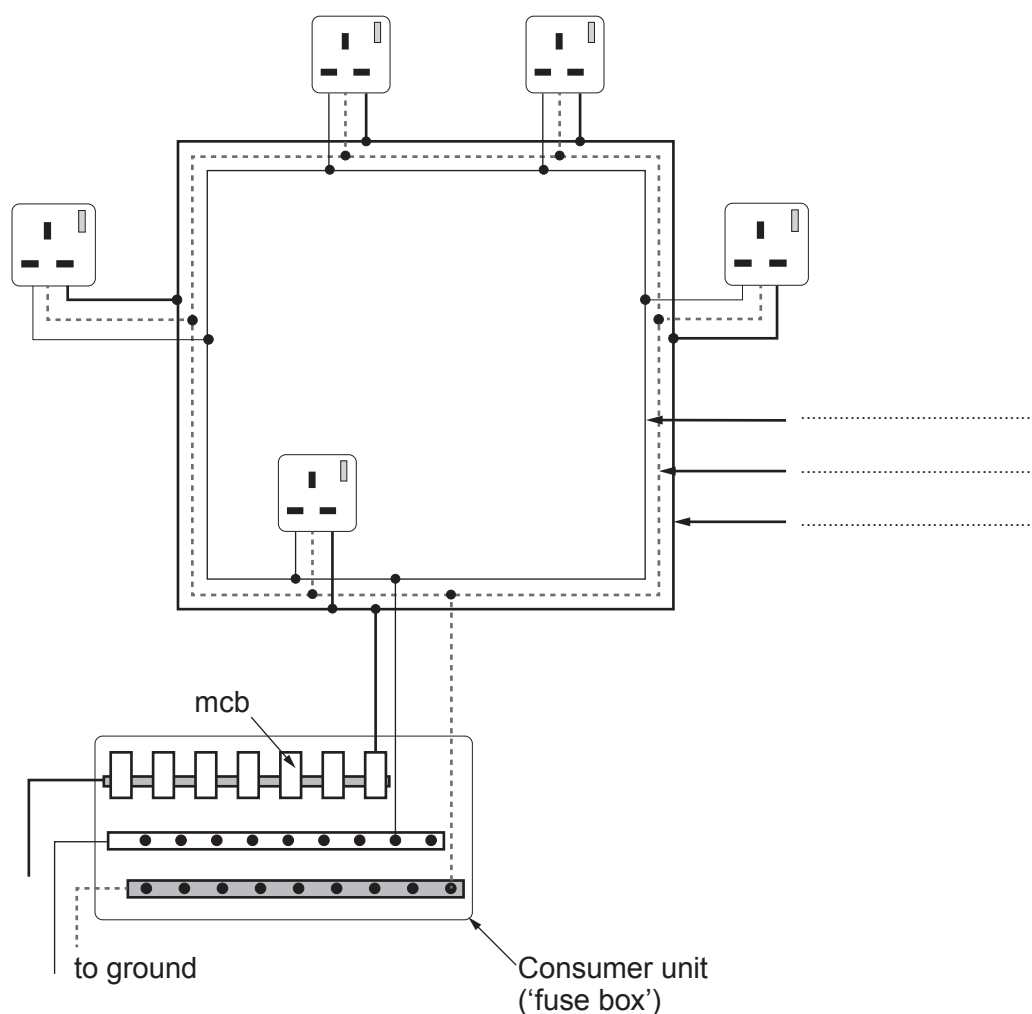


2. The diagram below shows a ring main circuit for a house.



(a) (i) **Label** the earth, neutral and live wires on the diagram above. [2]

(ii) Underline a word in each bracket to correctly complete the sentences below. [3]

The ring main is a looped (**double** / **parallel** / **series**) circuit. The cables in the ring main can be made (**thinner** / **thicker** / **longer**) because there are 2 paths for the (**voltage** / **current** / **power**).



Examiner
only

(b) A 1.2 kW kettle is plugged into the ring main. It is used for 0.5 hours in a day.
Use equations from page 2 to answer the following questions.

(i) Calculate the number of units (kWh) the kettle uses each day. [2]

Units used = kWh

(ii) Calculate the cost of using the kettle each day if electricity costs 15p per unit. [2]

Cost = p

9

