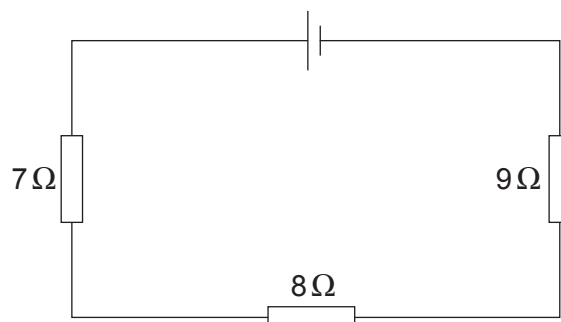


3. (a) The diagram shows three resistors connected in series.



- (i) Use an equation from page 2 to calculate the total resistance of the circuit. [1]

total resistance = Ω

- (ii) The battery voltage is 12 V.
Use an equation from page 2 to calculate the current in the circuit. [2]


current = A

- (iii) Use an equation from page 2 to calculate the power produced by the battery. [2]

power = W



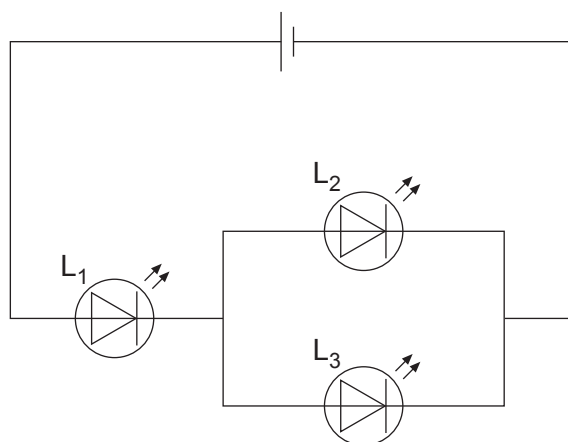- (b) The circuit below contains three **identical** components, L_1 , L_2 and L_3 , connected to a battery.



- (i) Tick (✓) the box next to the name of these components. [1]

Lamp

☐

LED

☐

LDR

☐

- (ii) The current in L_2 is 8 mA.

I. Write down the current in L_3 . current = mA [1]

II. Write down the current in L_1 . current = mA [1]

- (iii) I. State which **two** components (L_1 , L_2 or L_3) have the same voltage across them. [1]

..... and

II. State which **two** components (L_1 , L_2 or L_3) have voltages that add up to the battery voltage. [1]

..... and

