


6. A group of pupils investigate the current-voltage (I - V) characteristics of different components.

(a) The first component they investigate is a lamp.


Part of the circuit used is shown below.

Add a variable resistor **and** voltmeter to the circuit diagram.

[2]

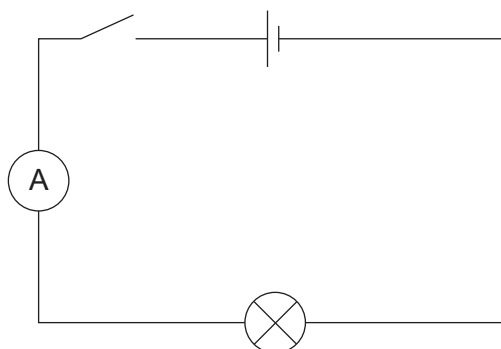

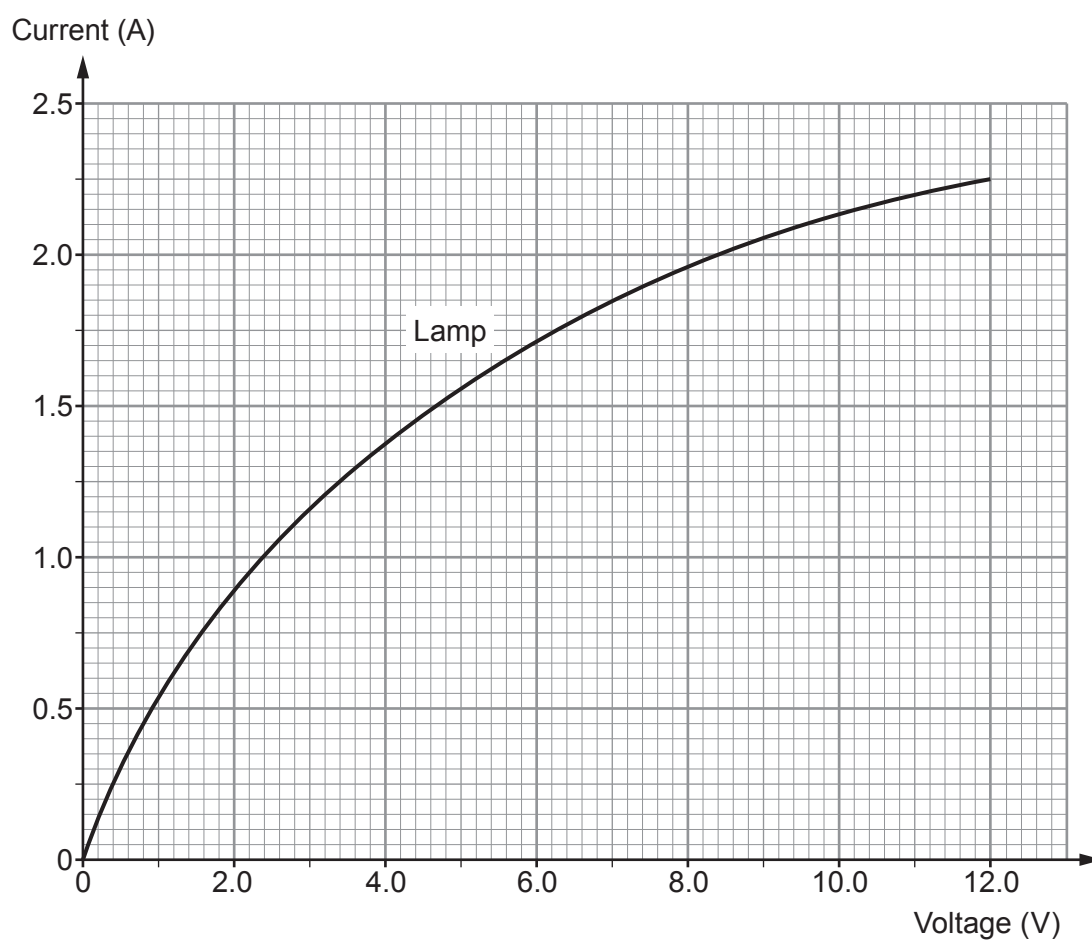(b) They draw a graph from their results for the **lamp**. It is shown below.



- (i) One student suggests that as the current through the lamp **doubles** the voltage **triples**.
Use pairs of data within the range 0.5 A to 2.0 A from the graph to explain whether you agree with the student. [3]
-
-

- (ii) Use the equation:

$$\text{power} = \text{voltage} \times \text{current}$$

and information from the graph to calculate the **maximum** power produced by the lamp. [3]

Power = W

- (c) The experiment is repeated with a $6\ \Omega$ resistor but the results are lost.

- (i) Use the equation:

$$\text{current} = \frac{\text{voltage}}{\text{resistance}}$$


to calculate the current through the $6\ \Omega$ resistor at 12 V. [2]

Current = A

- (ii) **Draw the line for this resistor** on the grid on the previous page. [1]



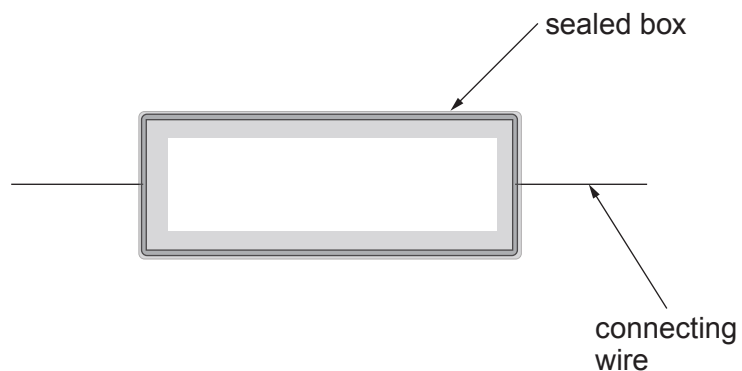- (d) The students are given a sealed box containing another component.



They are asked to confirm whether the hidden component is a diode.

- (i) Describe how they would use the circuit shown in part (a) to confirm whether or not it is a diode. [3]

.....


.....

.....

.....

.....

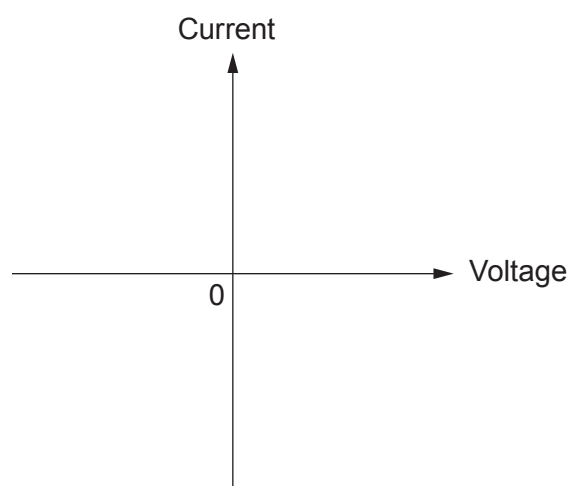- (ii) **Sketch** the I - V graph that you would expect to obtain for a diode on the grid below. [1]



END OF PAPER

