
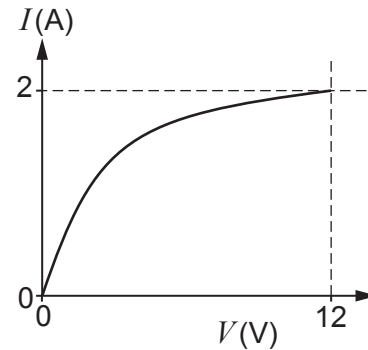


Examiner
only

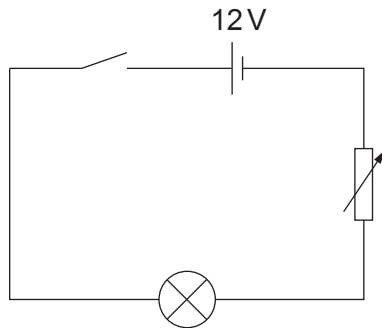2. Students set up the following circuit to investigate how the current through a 12V filament lamp varies with voltage.
Their results are shown on the graph.



- (a) Explain how they use the circuit to produce the results shown. Include in your answer:

- what additional components they need to add to the circuit
- how these components should be connected and what they are used for
- a method they can use to obtain several pairs of readings.

[6 QER]





(b) George states that the resistance of the lamp decreases as the voltage increases. Use the graph to explain whether you agree.

[2]

.....

.....

.....

Examiner
only

8

3430UC01
07

