

Question				Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
1.	(a)			Ammeter Don't accept ampmeter	1			1		1
	(b)	(i)		Point at (6.0 V, 0.7 A) circled	1			1		1
		(ii)		Straight line drawn with ruler with a < 1 small square tolerance, through all points including origin, but excluding anomaly Ignore any continuation of the line past 12 V		1		1	1	1
		(iii)	I	3.0 [A] ecf accept 3 [A]		1		1		1
			II	Substitution: $\frac{12.0}{3.0}$ ecf (1) = 4 [Ω] (1)	1	1		2	2	2
		(iv)		Resistance is constant / owtte		1		1		1
	(c)			Double (1) Half (1) Half (1)		3		3		3
				Question 1 total	3	7	0	10	3	10