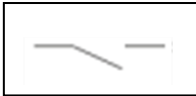
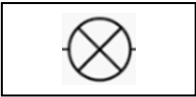
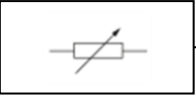
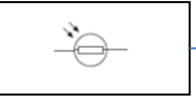


Question				Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
1	(a)			    lamp switch variable resistor LDR 4 correct – 3 marks 2 or 3 correct – 2 marks 1 correct – 1 mark	3			3		3
	(b)	(i)		Series (1) The same as (1)	2			2		2
		(ii)	I	Substitution: $P = 3 \times 0.25$ (1) $P = 0.75$ [W] (1) Accept 0.8 [W]	1	1		2	2	2
			II	Substitution: $R = \frac{3}{0.25}$ (1) $R = 12$ (1)	1	1		2	2	2

Question				Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
			III	Ω	1			1		1
	(c)			Decreases (1) Increases (1)	2			2		2
				Question 1 total	10	2	0	12	4	12