

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
6			Indicative content 1. Adjust the variable resistor. 2. Use the ammeter to measure the current. 3. Use the voltmeter to measure the voltage. 4. Record the readings of voltage and current. 5. Repeat steps 1 to 4 {for the full range of the variable resistor / to give several pairs of readings}. 6. Plot a graph of current (y-axis) against voltage (x-axis). 5 – 6 marks Detailed account of method. <i>There is a sustained line of reasoning which is coherent, relevant, substantiated and logically structured. The candidate uses appropriate scientific terminology and accurate spelling, punctuation and grammar.</i> 3 – 4 marks Partial account of method. <i>There is a line of reasoning which is partially coherent, largely relevant, supported by some evidence and with some structure. The candidate uses mainly appropriate scientific terminology and some accurate spelling, punctuation and grammar.</i>	6			6		6

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
			1–2 marks Limited account of method. Some points made from any parts of the indicative content. <i>There is a basic line of reasoning which is not coherent, largely irrelevant, supported by limited evidence and with very little structure. The candidate uses limited scientific terminology and inaccuracies in spelling, punctuation and grammar.</i> 0 marks <i>No attempt made or no response worthy of credit.</i>						
			Question 6 total	6	0	0	6	0	6