

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
7	(a)		450 [Ω]		1		1	1	
	(b)		Substitution: $\frac{1}{300} + \frac{1}{450}$ ecf (1) $\frac{1}{R} = \frac{5}{900}$ (1) = 180 [Ω] (1) Award 2 marks for 0.0055556 or 0.006 [Ω] Award 1 mark for 0.005 [Ω]	1	2		3	3	
	(c)		140 +180 ecf = 320 [Ω]		1		1	1	
			Question 7 total	1	4	0	5	5	0