

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
5 HT	(a)	(i)		All 4 points plotted correctly $\pm <1$ small square division (1) 1-3 points plotted correctly $\pm <1$ small square division (0) Straight line of best fit between 1.0 – 6.0 V within $\pm <1$ small square division of each point (1)		2		2	2	2
		(ii)		As the voltage increases, the current increases (1) at a decreasing rate (1) Award 2 marks - equal increases of voltage produce smaller increases in current Don't accept in a non-proportional way / the increase gets less steep / non-linearly		2		2	2	2
	(b)	(i)		Substitution: $\frac{3.0}{0.85}$ (1) = 3.53 [Ω] (1) Accept 3.5 [Ω] Don't accept 3.52 [Ω]	1	1		2	2	2
		(ii)		0.85 (1) i.e. denominator from (b)(i) + 0.6 ecf from graph = 1.45 [A] (1)		2		2	2	2
		(iii)		Substitution and recognition of total current I : $R = \frac{V}{I} = \frac{3.0}{1.45 \text{ ecf}}$ (1) = 2.07 [Ω] (1) Accept 2.1 or 2 [Ω] Alternative: $R_{\text{wire}} = \frac{V}{I} = \frac{3.0}{0.6 \text{ ecf}} = 5$ (1) then $\frac{1}{3.53 \text{ ecf}} + \frac{1}{5 \text{ ecf}} = 0.483$ so $R_{\text{total}} = 2.07$ [Ω] (1) Accept 2.1 or 2 [Ω]		2		2	2	2
		(iv)		By having two loops from the battery there is more current (1) Greater current implies smaller resistance (1)	2			2		2

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
		(v)		The current through the lamp is smaller than the current through the resistor or values stated 1.2 [A] for the resistor and 1.125 [A] for the lamp (1) [Since the voltage is the same] bigger resistance results in a smaller current (1) Alternative: calculations based $R = 5\text{ }[\Omega]$ for wire (1) and $R = 5.33\text{ }[\Omega]$ for lamp (1) Don't accept reference to gradients		2		2	2	2
		(vi)		Any 2 × (1) from: - At 5.50 V or where the lines cross [the currents are equal so] the powers are equal $[I_{\text{resistor}} \text{ is less than } I_{\text{lamp}}]$ up to 5.50 V, therefore $P_{\text{lamp}} > P_{\text{resistor}}$ (since voltages are the same and $P=VI$) - Beyond 5.50 V, $[I_{\text{resistor}} \text{ is greater than } I_{\text{lamp}} \text{ therefore}] P_{\text{lamp}} < P_{\text{resistor}}$		2		2	2	2
				Question 5 total	3	13	0	16	14	16