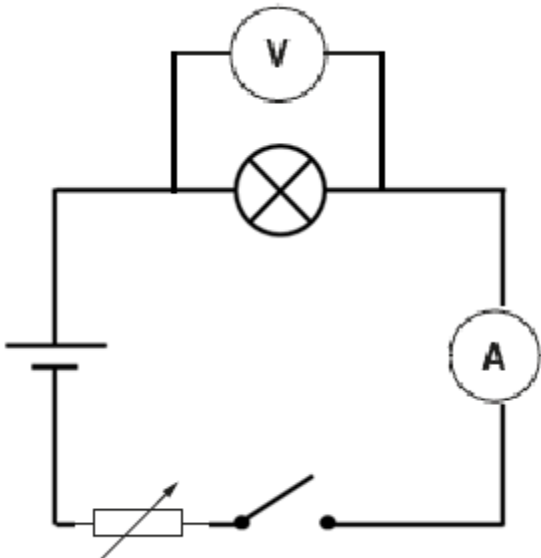


Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
6 FT 1 HT	(a)	(i)		Variable resistor in series (1) Ammeter in series (1) Voltmeter in parallel across lamp (1) 	3			3		3
		(ii)		Variable resistor set at maximum/minimum value (1) I <u>and</u> V values measured (1) Resistance of variable resistor varied and new values recorded (1)						