

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
5 HT	(a)			Total resistance = $8 + 4 = 12$ (1) $I = \frac{12}{12 \text{ (ecf)}}$ (1) $= 1 \text{ A}$ (1)		3		3	3	
	(b)	(i)		$\frac{1}{R_1} = \frac{1}{12} + \frac{1}{8} = \frac{5}{24}$, so $R_1 = 4.8$ (1) $\frac{1}{R_2} = \frac{1}{4} + \frac{1}{6} = \frac{5}{12}$, so $R_2 = 2.4$ (1) total resistance = $4.8 + 2.4 = (7.20 \text{ } [\Omega])$ (subs) (1) (ecf) (ecf)	1	2		3	3	
		(ii)		Current = $\frac{12}{7.2} = 1.67$ (1) (allow ecf for 7.2) Current splits $\frac{2}{3}$ (1) Power = $\frac{4}{9} \times 12 = 5.33 \text{ W}$ (1) Alternative Current = $\frac{12}{7.2} = 1.67$ (1) (allow ecf for 7.2) Pd across first parallel $1.67 \text{ (ecf)} \times 4.8 \text{ (ecf)} = 8.016$ I in $12 \text{ } \Omega$ resistor is $\frac{8.016}{12} \text{ (ecf)} = 0.668 \text{ A}$ (1) $P = I^2 R = 5.35 \text{ [W]}$ (1)		3		3	3	
				Question 5 total	1	8	0	9	9	0