

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
4	(a)	(i)		Correct positioning of ammeter (1) and voltmeter (1)	2			2		2
		(ii)		Current = $12 / 800$ (subs and selection) = 0.015A (1)		2		2	2	
		(iii)		From 2 to 4 cm – resistance doubles from 400 to 800 (1) But for the others distances e.g. from 4 - 6 and 6 - 8 – resistance does not double quoting data from table so claim is incorrect (1)			2	2		
	(b)			Stayed the same		1		1		
				Question 4 total	2	3	2	7	2	2