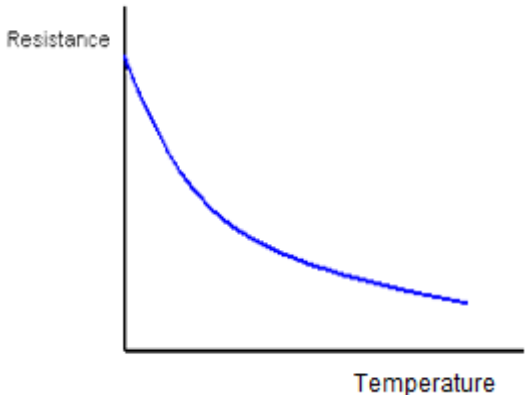


Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
7	(a)	(i)		 Resistance Temperature	1			1		1
		(ii)		or alternative graph of resistance increasing with temperature thermistor resistance decreases (1) total resistance decreases (1) So ammeter reading increases (1) So voltage across R increases (1) Therefore voltmeter reading decreases (1) Allow converse statements which are linked to candidates graph If alternative graph is used – accept the following thermistor resistance increases (1) total resistance increases(1) So ammeter reading decrease (1) So voltage across R decrease (1) Therefore voltmeter reading increase (1) Answer should link to candidate graph	1	4		5		4