

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
3.				Indicative content: Series circuit the current is the same through the circuit Current $A1 = A2 = A3$ / lamps the same brightness the total voltage is the sum of the voltages across each component Voltage $V1 = V2 + V3$ $V2 = V3$ voltages smaller than in parallel circuit Parallel circuit In a parallel circuit, the total current before it splits at a junction equals the sum of the currents in the branches Current $A1 = A2 + A3$ The voltage across each component in parallel is the same $V2 = V3$ Accept $V1$ equal on both circuits (don't accept $A1$ equal) Accept greater power output from parallel 5-6 marks At least 5 valid points from either circuit – there must be correct reference to both circuits <i>There is a sustained line of reasoning which is coherent, relevant, substantiated and logically structured. The candidate uses appropriate scientific terminology and accurate spelling, punctuation and grammar.</i> 3-4 marks At least 3 valid points from either circuit <i>There is a line of reasoning which is partially coherent, largely relevant, supported by some evidence and with some structure. The candidate uses mainly appropriate scientific terminology and some accurate spelling, punctuation and grammar.</i>	6			6		6