

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
6.	(a)	(i)	I	the resistance in the parallel circuit is smaller (1) by $4 \times$ (1) Accept converse answer Accept 'it' as parallel OR Total resistance in series circuit = $2 \times R_1$ (1) Total resistance in parallel circuit = $R_1/2$ (1) OR The total parallel resistance is $4.5/4$ (1) $=1.125$ (1)		2		2		3
			II	parallel is ($4 \times$) bigger than series OR Current is 8 A		1		1		
		(ii)		The voltmeter reading in the parallel circuit is more (1) by $2 \times$ (than the series circuit) (1) OR Voltmeter reading is 9V in parallel (1) 4.5 V in series (1) OR The voltage is shared in series / not shared in parallel (1) So voltmeter reading is bigger in parallel (1)		2		2		1