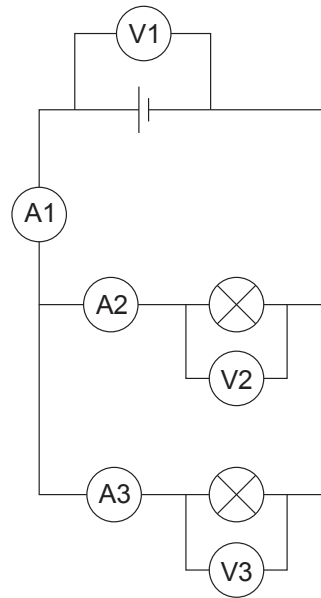


Examiner
only

parallel circuit



- the readings on the ammeters
- the readings on the voltmeters.

[6 QER]