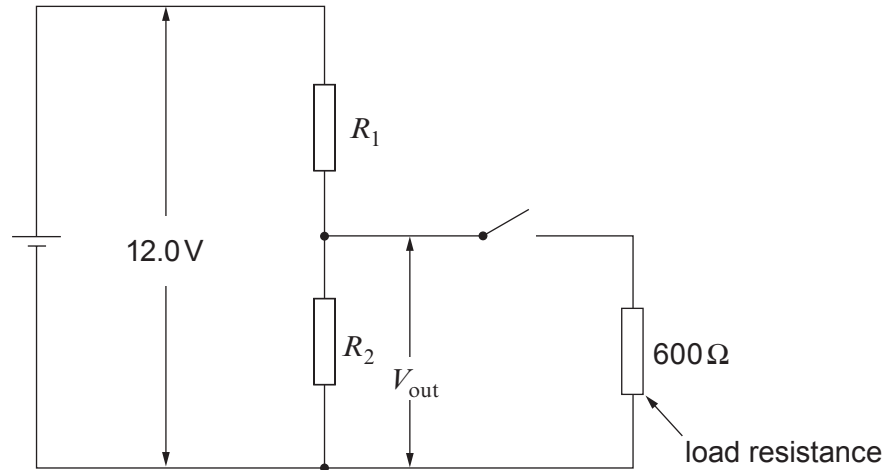


3. For the potential divider circuit shown a student is asked to select values for R_1 and R_2 so that the circuit meets certain requirements.



Requirements

- A** an output pd, V_{out} , of 3.0V when unloaded (switch open),
- B** a power dissipation of less than 0.50W in R_1 when unloaded (switch open),
- C** a **decrease** of less than 0.40V in V_{out} when the switch is closed.

Showing your working clearly, determine whether or not the circuit meets the requirements when $R_1 = 450\Omega$ and $R_2 = 150\Omega$.

- (a) Requirement **A**: an output pd, V_{out} , of 3.0V when unloaded (switch open). [2]

.....

.....

.....

.....

- (b) Requirement **B**: a power dissipation of less than 0.50W in R_1 when unloaded (switch open). [2]

.....

.....

.....



(c) Requirement **C**: a **decrease** of less than 0.40V in V_{out} when the switch is closed. [4]

.....

.....

.....

.....

.....

.....

.....

.....

8

2420U201
07