

2. (a) A battery does not *store* charge. State what a battery *does* do in relation to charge in an electric circuit. [1]

.....

.....

- (b) A battery consists of three cells, **each** of emf 1.60V and internal resistance 0.10Ω , connected in series. The battery is connected to an electromagnet of resistance 1.20Ω .

- (i) Show clearly that the current is approximately 3A. [The space is for a diagram if required.] [3]

.....

.....

.....

.....

- (ii) Calculate the rate (in watts) at which:

- I. energy is dissipated by the electromagnet; [1]

.....

.....

- II. the battery's chemical energy is being used. [1]

.....

.....

- (iii) The answer to (b)(ii)II. is expected to be greater than the answer to (b)(ii)I. Explain where the missing energy goes. [2]

.....

.....

.....



- (c) A student wishes to maximise the current through the electromagnet. She has a spare cell of emf 1.50 V and internal resistance $0.50\ \Omega$. Evaluate whether or not she should put it in series with the battery, giving your calculations and conclusion clearly. [2]

.....

.....

.....

.....

.....

10

2420U201
05