
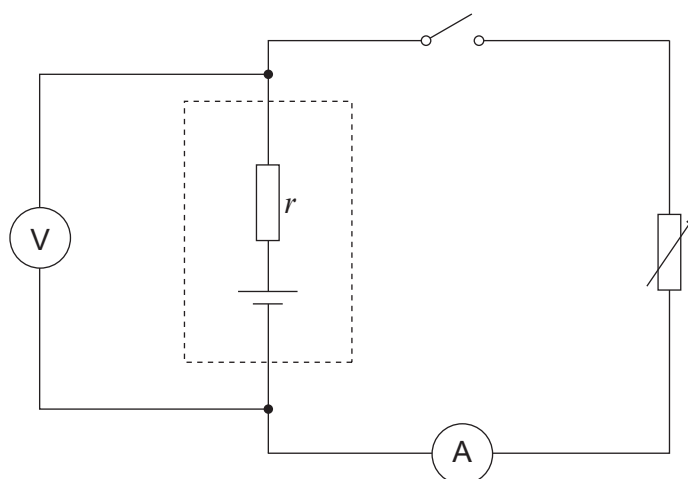


Answer **all** questions.

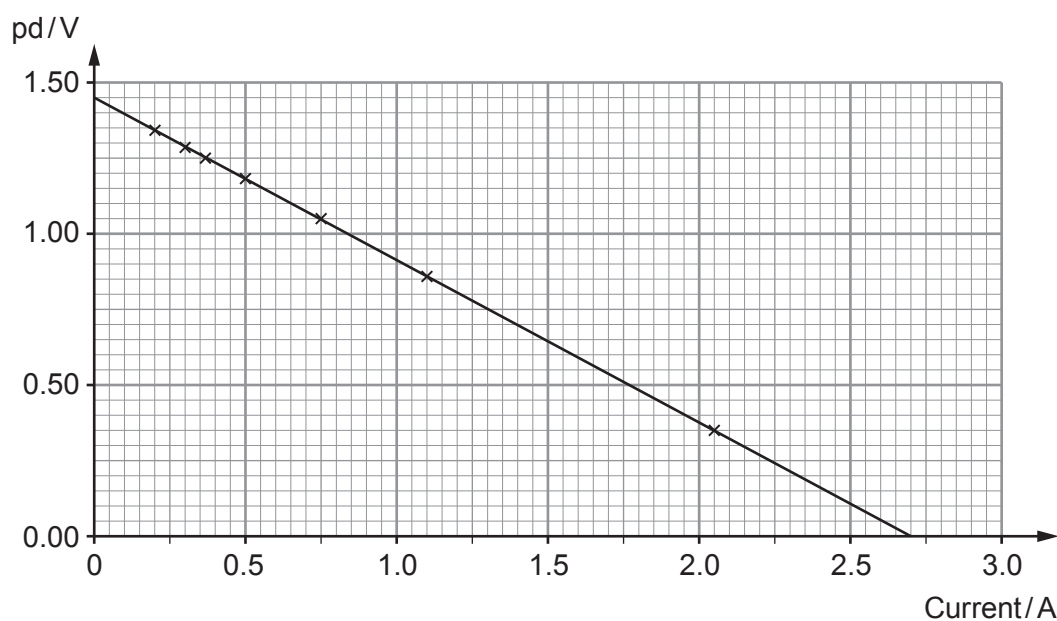1. Anwen sets up the circuit shown in order to investigate a cell. The variable resistor is adjusted and readings are obtained from the voltmeter and ammeter.



The readings are plotted as shown.



- (a) The manufacturer claims that the emf of the cell is 1.50 V. Explain, in terms of energy, what this statement means. [2]

.....

.....

.....



- (b) An equation applying to a cell of emf, E , and internal resistance, r , is:

$$V = E - Ir$$

- (i) Explain how Anwen's graph is in good agreement with this equation. [2]

.....

.....

.....

- (ii) Calculate the gradient of the line and hence determine a value for the cell's internal resistance. [2]

.....

.....

.....

- (iii) Evaluate the manufacturer's claim that the emf is 1.50 V. [1]

.....

.....

- (c) (i) Use the graph to determine the greatest current the cell can supply. [1]

.....

- (ii) State the resistance of the variable resistor when the current is at its maximum. [1]

.....

