

3. A battery has an emf of 12 V.

- (a) (i) Explain what this statement means.

[2]

.....

.....


- (ii) State why it is usually a disadvantage for a battery to have an internal resistance.

[1]

.....

.....

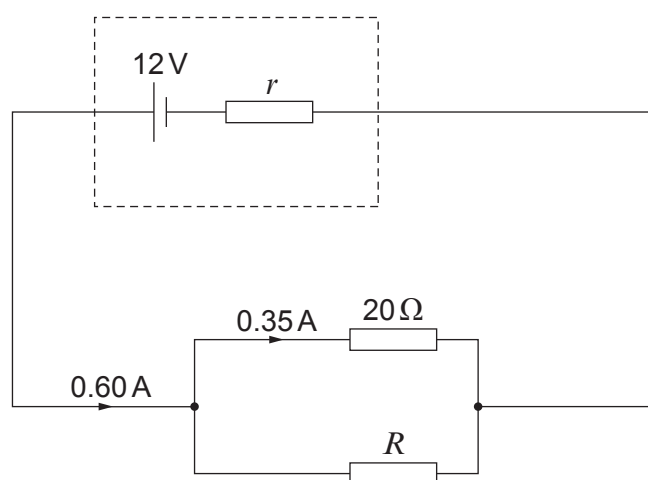- (b) The battery is included in the circuit shown.



- (i) Use the information shown on the circuit diagram to calculate:

- I. the resistance, R .

[2]

.....

.....

.....

- II. the internal resistance, r .

[2]

.....

.....

.....



- (ii) I. Calculate the energy transferred in the $20\ \Omega$ resistor in 40 minutes. [2]

.....

.....

.....

- II. State the energy transfer that occurs in the $20\ \Omega$ resistor and explain, in terms of the motion of free electrons, how it takes place. [2]

.....

.....

.....

- (iii) Dafydd claims that if R is replaced by a higher resistance, but no other changes are made, the power dissipation **in the $20\ \Omega$ resistor** will increase. Evaluate this claim, showing clear reasoning. [3]

.....

.....

.....

.....

.....

.....

