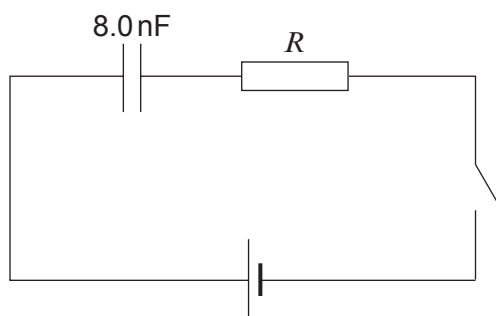



- (c) An identical, uncharged 8.0 nF capacitor is **charged** in the following circuit, **using the same large resistor, R** . The switch is closed and the capacitor is uncharged at time $t = 0$.



Without further calculations, sketch graphs of:

- (i) the charge on the plates of the capacitor against time;

[2]

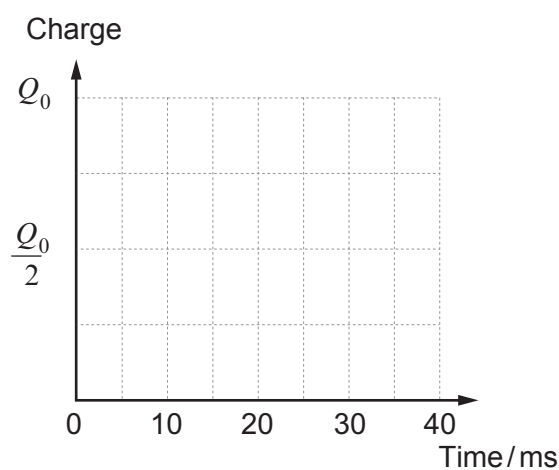

- (ii) the current in the circuit against time.

[2]

