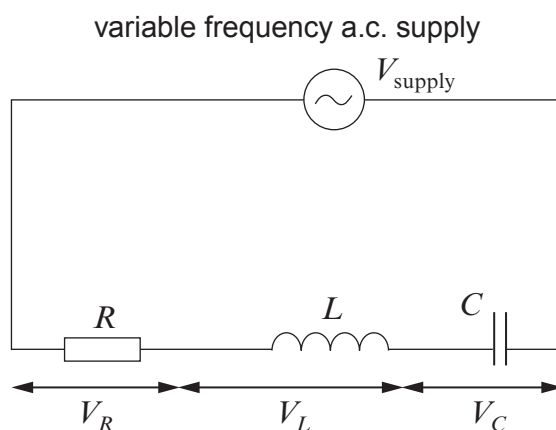


Option A – Alternating Currents

6. (a) The following *RCL* circuit is constructed.



For this *RCL* circuit, describe the relationships between the rms pds V_{supply} , V_R , V_L and V_C :

- (i) when the circuit is not in resonance;
Space for diagram.

[3]

.....

.....

.....

.....

.....

.....

.....

- (ii) when the circuit is in resonance.

[2]

.....

.....

.....

.....


.....

.....

.....



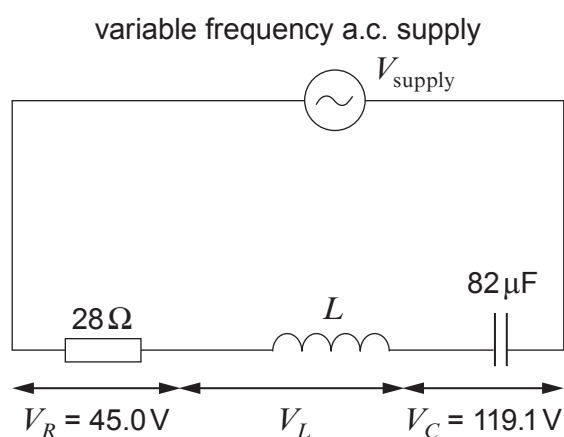- (b) The following *RCL* circuit is **at resonance**. The values of *R* and *C* are provided along with their rms pd values.



Calculate:

- (i) the *Q* factor of the circuit; [1]

.....

.....

- (ii) the rms current; [1]

.....

.....

- (iii) the frequency of the power supply; [2]

.....

.....

.....

.....

- (iv) the inductance of the inductor. [2]

.....


.....

.....

.....



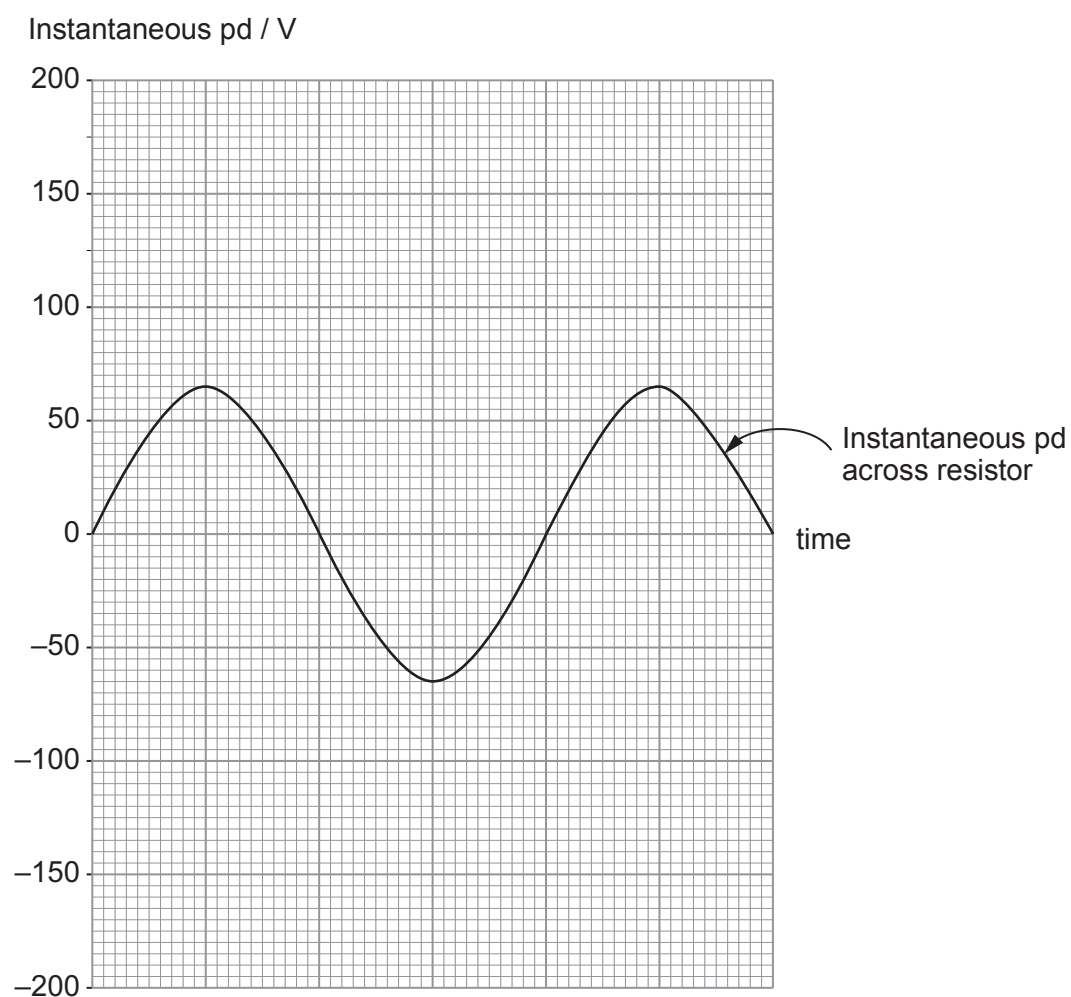- (v) Sketch a graph of the instantaneous pd across the capacitor on the grid provided. (The instantaneous pd across the resistor is shown.) [2]



- (vi) Without further calculation, explain why the current decreases when the frequency of the power supply is increased. [2]

.....

.....

.....

.....



- (c) Sam claims that the output pd (V_{OUT}) in the following circuit is greater than 6.0 V when the frequency is greater than 20 kHz, but less than 6.0 V when below 20 kHz. Investigate whether or not Sam is correct. [5]

