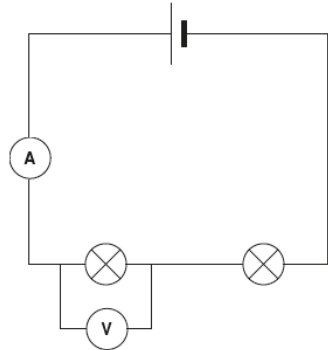


Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
2 FT	(a)	(i)		Series (1) the same as (1)	2			2		
		(ii)		Parallel (1) the same as (1)	2			2		
	(b)	(i)		Total resistance = $3 + 3 = 6$ (1) Substitution $\frac{9}{6\text{ (ecf)}}$ (1) = 1.5 (1) Do not accept $\frac{9}{3} = 3$	1	1 1		3	3	3
		(ii)		Doubles Accept increase Accept a calculation to show this			1	1	1	1
	(c)			9×3 Subs (1) = 27 (1)	1	1		2	2	
	(d)			D 	1			1		1
	(e)			Any $2 \times (1)$ from: Brighter lamps (1) if one breaks others still work / switched on independently(1) they will have the same voltage (1)	2			2		
				Question 2 total	9	3	1	13	6	5