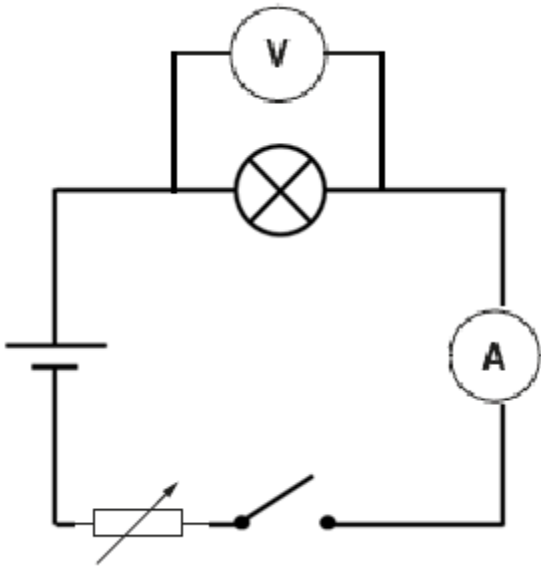


Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
6 FT 1 HT	(a)	(i)		Variable resistor in series (1) Ammeter in series (1) Voltmeter in parallel across lamp (1) 	3			3		3
		(ii)		Variable resistor set at maximum/minimum value (1) I <u>and</u> V values measured (1) Resistance of variable resistor varied and new values recorded (1)						

Question				Marking details	Marks Available					
					AO1	AO2	AO3	Total	Maths	Prac
	(b)	(i)		6 correct plots <1 square tolerance (2) 5 correct plots <1 square tolerance (1) less than 5 correct plots (0) Smooth curve of best fit through points that candidates have plotted from 2,0.8 point onward(1) Do not accept thick, wispy, disjointed lines or point to point		3		3	3	3
		(ii)		As V increases I increases at a decreasing rate.		2		2		2
	(c)	(i)		Selection of correct current of 0.5 [A] (1) Answer = 1 [Ω] (1) accept correct answer for 2 marks		2		2		
		(ii)		increases			1	1		
	(d)	(i)		Subs of 0.5×0.5 (1) = 0.25[W] (1)	1	1		2	2	
		(ii)		increases			1	1		
	(e)			Diagonal straight line to origin (1) to 12,1.5 or point indicated(1)		2		2	2	2
				Question 6 total	7	10	2	19	7	13