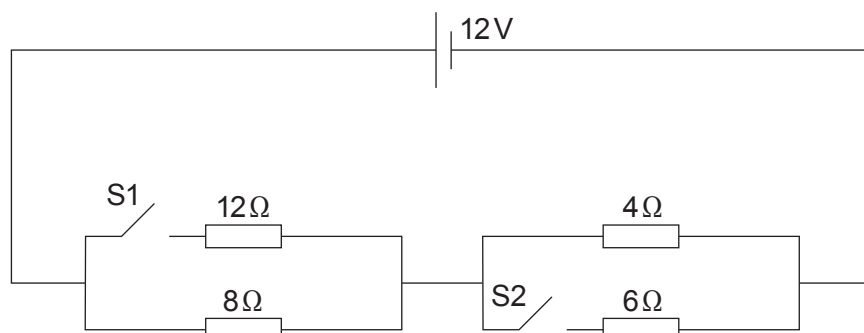


5. Students investigated the following electrical circuits.



Select the appropriate equations to answer the following questions.

voltage = current $\times$ resistance

$$R = R_1 + R_2$$

power = current² $\times$ resistance

$$\frac{1}{\text{total resistance}} = \frac{1}{\text{total resistance X}} + \frac{1}{\text{total resistance Y}}$$

(a) Calculate the current supplied when both switches are open.

[3]

Current = A

(b) (i) Calculate the total resistance in the circuit.

[3]

Total resistance = Ω

- (ii) Calculate the power dissipated as heat by the 12Ω resistor.

[3]

Examiner
only

Power = W

9