

6. Jamie is investigating series and parallel electrical circuits.

The following equations apply to electrical circuits:



$$\text{current} = \frac{\text{voltage}}{\text{resistance}}$$

$$\text{power} = \text{voltage} \times \text{current}$$

$$\text{power} = \text{current}^2 \times \text{resistance}$$

$$R_T = R_1 + R_2 \dots\dots\dots$$
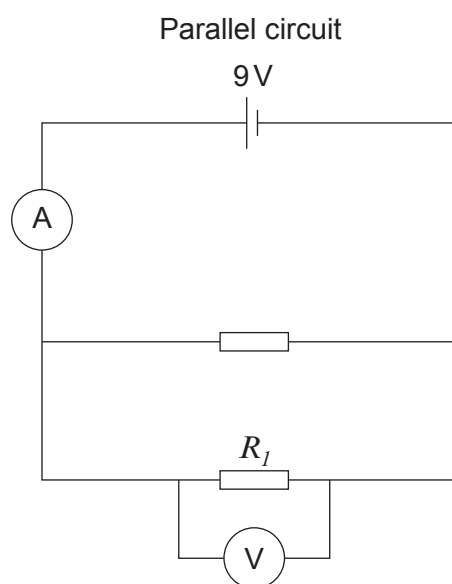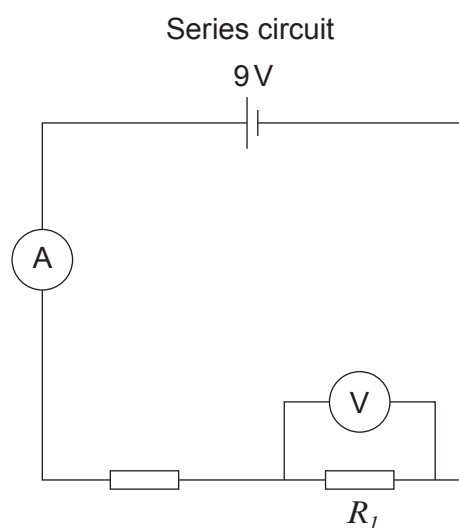
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \dots\dots\dots$$



- (a) Jamie built the circuits above with identical resistors. In the series circuit the total resistance is 4.5 ohms and the ammeter reading is 2 Amps.

- (i) I. Compare the total resistance in the parallel circuit with the series circuit. [2]

.....

.....



II. Compare the ammeter reading in the parallel circuit with the series circuit. [1]

(ii) Explain how the voltmeter readings in the two circuits compare. [2]

(iii) Explain how the power dissipated in resistor R_I in each circuit compares. [2]

(b) Jamie used identical 2.25Ω resistors in both circuits.

(i) Calculate the power dissipated by R_I in the parallel circuit. [4]

power dissipated = W

(ii) Use your answer above to calculate the power dissipated in resistor R_I in the series circuit. [2]

power dissipated = W

