

Question			Marking details	Marks available				Maths	Prac
				AO1	AO2	AO3	Total		
1	(a)	(i)	Capacitor equation rearranged $\frac{Cd}{\epsilon_0} = A$ (1) Area = x^2 used (1) Correct answer = 42.5 [cm] (1)	1	1				
		(ii)	Logical method employed e.g. eliminating 1, 2 etc.(can be implied by correct calculation for 4) (1) Evidence of a correct capacitor in series calculation (1) Evidence of a correct capacitor in parallel calculation (1) Number 4 chosen (1)		1		3	3	
		(iii)	Dielectric / increase the permittivity Accept a named dielectric	1		4	4	2	
		(iv)	Valid method e.g. $\frac{q^2}{2C} = U$ or 2 other valid equations (1) Accept use of 3 equations Rearrangement or algebra (1) Answer = 9.96×10^{-8} [C] (accept 1×10^{-7} C) (1)	1					
	(b)	(i)	RC used as the time constant (1) Answer = 1.94 M[Ω] (1)	1	1		2	2	
		(ii)	2 time constants interpreted or substitution into: $q = q_0 e^{-t/CR}$ (1) 0.37 ² or rearrangement of equation ecf (1) Answer = 0.135 or 13.5% or $\frac{27}{200}$ (1)		3		3	3	
	(c)	(i)	Correct shape (starting from 0,0 increasing with decreasing gradient) (1) 50-75% charged at 15.5 ms or 8-15 ms half-life (1)	1	1		2	2	2
		(ii)	Correct shape (starting from I_0 , 0 decreasing and decreasing negative gradient) (1) 50-75% discharged at 15.5 ms or 8-15 ms half-life (1)	1	1		2	2	2
			Question 1 total	6	10	4	20	17	4