

SECTION B

Option A – Alternating Currents

| Question |     |       | Marking details                                                                                                                                                                                                                                                               | Marks available |     |     |       |       |      |
|----------|-----|-------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|-----|-----|-------|-------|------|
|          |     |       |                                                                                                                                                                                                                                                                               | AO1             | AO2 | AO3 | Total | Maths | Prac |
| 7        | (a) | (i)   | Choosing correct equation ( $\omega BAN$ ) (1)<br>Correct answer = 421 [V] (1)                                                                                                                                                                                                | 1               | 1   |     | 2     | 1     |      |
|          |     | (ii)  | Choosing correct equation ( $BAN \cos \omega t$ ) (1)<br>Answer = 0 <b>or</b> close to 0 (1)<br>Award 1 mark for answer of 1.34                                                                                                                                               | 1               | 1   |     | 2     | 1     |      |
|          |     | (iii) | 421 [V] <b>ecf</b> from (i)                                                                                                                                                                                                                                                   |                 | 1   |     | 1     | 1     |      |
|          |     | (iv)  | Period is 20 ms so 5 ms quarter cycle (1)<br>$\omega t$ is 90° or equivalent (1)<br>Expect max emf and zero flux (1)<br><br><b>Alternative:</b><br>$\omega t$ is 90° or equivalent (1)<br>$\cos 90^\circ = 0$ and $\sin 90^\circ = 1$ (1)<br>Expect max emf and zero flux (1) |                 |     | 3   | 3     |       |      |
|          | (b) | (i)   | Choosing correct equation i.e. $\frac{1}{2\pi} \sqrt{\frac{1}{LC}}$ (1)<br>Answer = 103 k[Hz] (1)                                                                                                                                                                             | 1               | 1   |     | 2     | 1     |      |

| Question |  |       | Marking details                                                                                                                                                                                                                                | Marks available |                 |          |           |           |          |
|----------|--|-------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|-----------------|----------|-----------|-----------|----------|
|          |  |       |                                                                                                                                                                                                                                                | AO1             | AO2             | AO3      | Total     | Maths     | Prac     |
|          |  | (ii)  | Both reactances cancel <b>or</b> total impedance is $R$ <b>or</b> equivalent (1)<br>$I = \frac{V}{Z} = \frac{V}{R}$ (or equivalent) (1)                                                                                                        | 1               | 1               |          | 2         |           |          |
|          |  | (iii) | Any correct reactance ( $X_C = 10\,105$ , $X_L = 10\,556$ ) (1)<br>Impedance correctly obtained $485\, [\Omega]$ (1)<br>Substitution into $I = \frac{V}{Z}$ <b>ecf</b> on $Z$ (1)<br>Correct answer = $5.15\, \text{mA}$ <b>ecf</b> on $Z$ (1) | 1               | 1<br>1<br><br>1 |          | 4         | 4         |          |
|          |  | (iv)  | Large decrease in current or $\frac{\Delta I}{\Delta f}$ (1)<br>For small increase in frequency or is large (1)                                                                                                                                | 1               | 1               |          | 2         | 2         |          |
|          |  | (v)   | Realising $\omega$ also changes <b>OR</b> using / deriving $\frac{1}{R}\sqrt{\frac{L}{C}}$ (1)<br>Correctly linking valid equation to obtain yes <b>OR</b> simply yes<br>e.g.in $\frac{\omega L}{R}$ $\omega$ decreases so yes (1)             |                 |                 | 2        | 2         |           |          |
|          |  |       | <b>Question 7 total</b>                                                                                                                                                                                                                        | <b>6</b>        | <b>9</b>        | <b>5</b> | <b>20</b> | <b>10</b> | <b>0</b> |