Examiner only

6. Describe how the current-voltage $(I\text{-}V)$ characteristic of a filament lamp can be investigated using the following circuit. [6 QER]

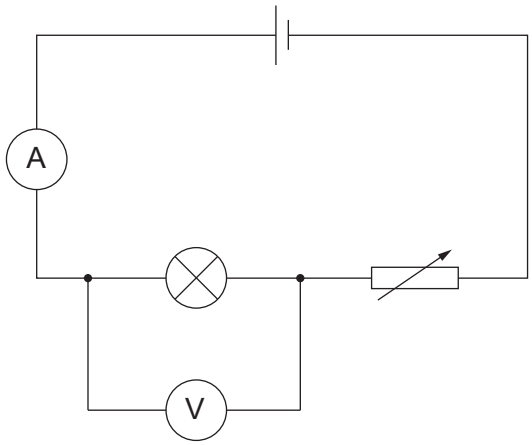

6

© WJEC CBAC Ltd.