Examiner only

(b) A group of students investigated the **charging** of a capacitor through a resistor and obtained the following data.

pd across capacitor / V

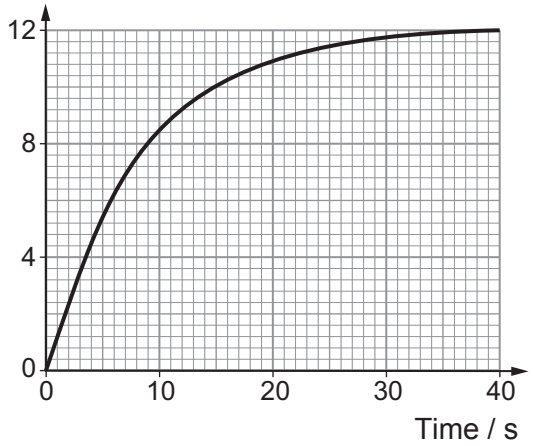

Current / mA

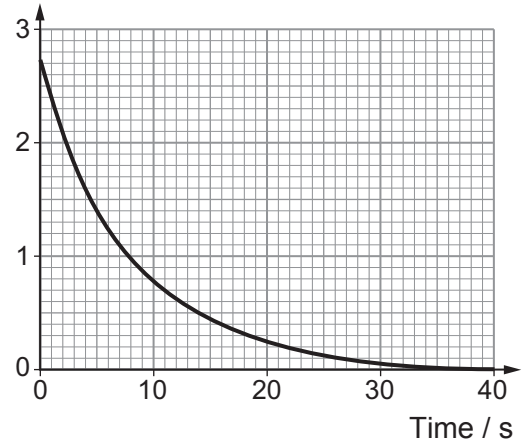

(i) Draw a circuit diagram of the apparatus that might have been used to obtain the data. [2]

(ii) Use the graphs to determine:

- the emf of the power supply;
- the resistance of the resistor;
- the capacitance of the capacitor. [5]

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

18

© WJEC CBAC Ltd.