Examiner only

3. The two circuits below are often used in a school laboratory. The lamps are identical.

series circuit

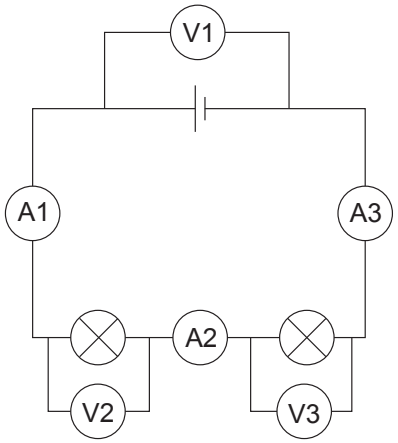

parallel circuit

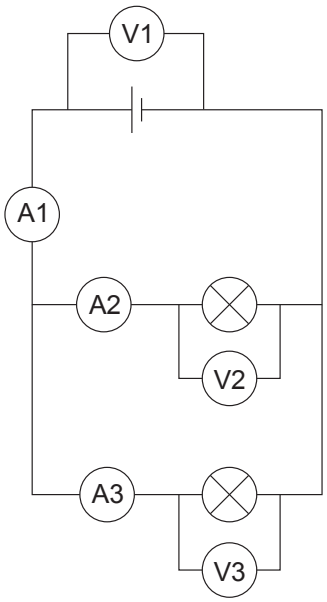

For each circuit compare:
- the readings on the ammeters
- the readings on the voltmeters.

[6 QER]

6

© WJEC CBAC Ltd.